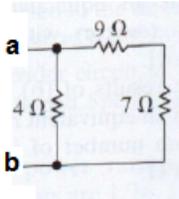


**Part I. Drills -- 1 point each**

Find the equivalent resistance measured at terminals a and b. Remember all currents in a series path are the same. All voltages across parallel paths are the same.


1)



$$R = 4 \parallel (9+7)$$

$$= \frac{4 \cdot 16}{4+16} = \underline{\underline{3.2 \Omega}}$$


2)

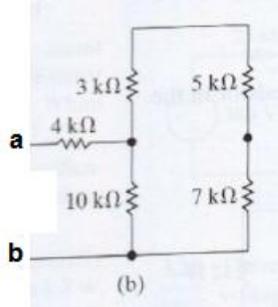

$$R_{ab} = 4 + 10 \parallel (3+5+7)$$

$$= 4 + \frac{10 \cdot 15}{10+15} = 4 + 6 = \underline{\underline{10 k \Omega}}$$

3)

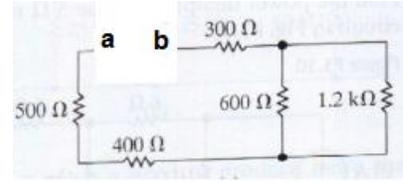


$$R_{ab} = 500 + 400 + 600 \parallel (1200 + 300)$$

$$= 1200 + \frac{600 \cdot 1200}{1800} = 1200 + 900 = \underline{\underline{1600 \Omega}}$$

4) Use voltage division to find the voltages  $v_0$  and  $v_1$


a) This is Prob 2.27 in your text

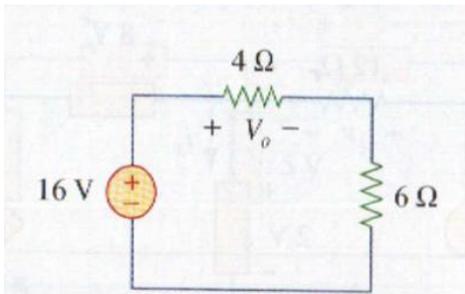

Using voltage division,

$$V_o = \frac{4}{4+16}(16V) = \underline{\underline{6.4 V}}$$

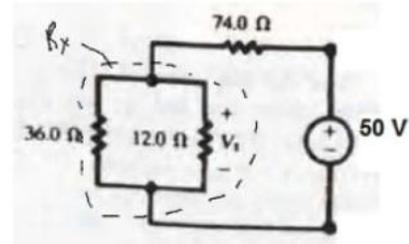b) Note  $V_1$  is measured across the  $36 \parallel 12$  combination




$$R_x = 12 \parallel 36 = 9 \Omega$$

$$V_1 = \frac{50 \cdot 9}{9+74} = \underline{\underline{5.42 V}}$$


5) Find the current  $i$  using current division

a.

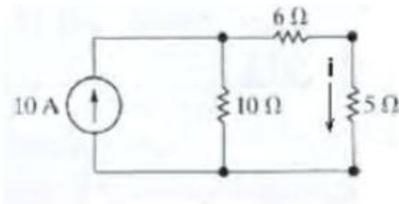

$$i = \frac{10A \cdot 10 \Omega}{(10 + 11) \Omega} = \underline{\underline{4.76 A}}$$

b.

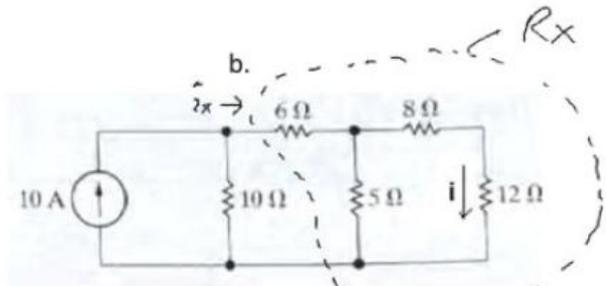


$$R_x = 6 + 5 \parallel (8+12)$$

$$= 6 + \frac{5 \cdot 20}{25} = 6 + 4 = 10 \Omega$$


$$i_x = \frac{10A \cdot 10 \Omega}{(10+10) \Omega} = 5A, \quad i = \frac{i_x \cdot 5}{5+8+12} = \frac{25}{25} = \underline{\underline{1A}}$$

6) Convert the Wye to Delta and the Delta to Wye

a. this is 2.48a

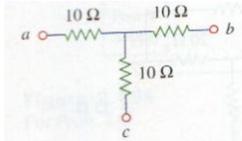

b. this is 2.49a

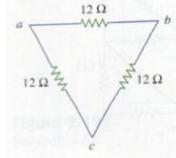

(a)  $R_a =$   

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{100 + 100 + 100}{10} = 30$$


$$R_a = R_b = R_c = \underline{30 \Omega}$$

(a)  $R_1 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{12 * 12}{36} = 4 \Omega$   

$$R_1 = R_2 = R_3 = \underline{4 \Omega}$$

Part II. Assisted Problem Solving – 2 pts each

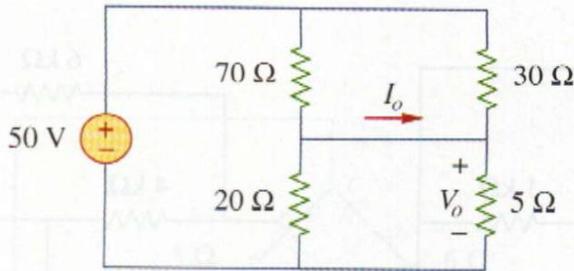2.35 Calculate  $V_o$  and  $I_o$  in the circuit



Combining the versions in parallel,

$$70 \parallel 30 = \frac{70 \times 30}{100} = 21 \Omega, \quad 20 \parallel 5 = \frac{20 \times 5}{25} = 4 \Omega$$

$$i = \frac{50}{21 + 4} = 2 \text{ A}$$

$$v_i = 21i = 42 \text{ V}, \quad v_o = 4i = 8 \text{ V}$$


$$i_1 = \frac{V_1}{70} = 0.6 \text{ A}, \quad i_2 = \frac{V_2}{20} = 0.4 \text{ A}$$

At node a, KCL must be satisfied

$$i_1 = i_2 + I_o \rightarrow 0.6 = 0.4 + I_o \rightarrow I_o = 0.2 \text{ A}$$

Hence  $v_o = \underline{8 \text{ V}}$  and  $I_o = \underline{0.2 \text{ A}}$

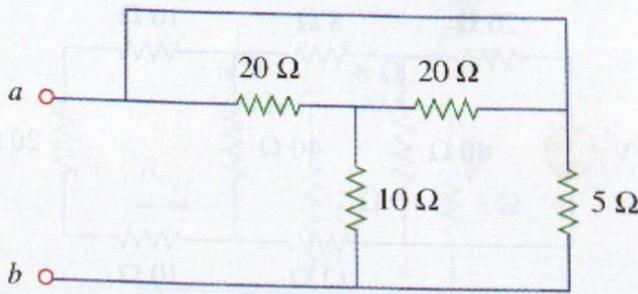2.44 For the circuit obtain the equivalent resistance at terminals a-b.




Convert Y to Delta to obtain

$$R_1 = \frac{20 \times 20 + 20 \times 10 + 10 \times 20}{10} = \frac{800}{10} = 80 \Omega$$

$$R_2 = \frac{800}{20} = 40 \Omega = R_3$$


The circuit becomes that shown below.

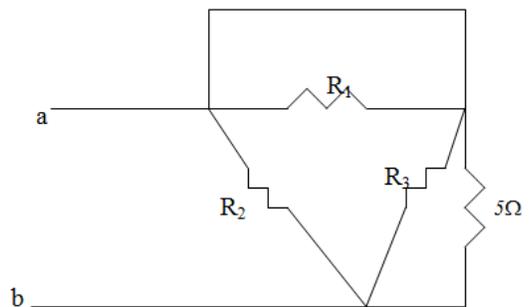


$$R_1 // 0 = 0, \quad R_3 // 5 = 40 // 5 = 4.444 \Omega$$

$$R_{ab} = R_2 // (0 + 4.444) = 40 // 4.444 = \underline{4 \Omega}$$

9) Find V in the following circuit

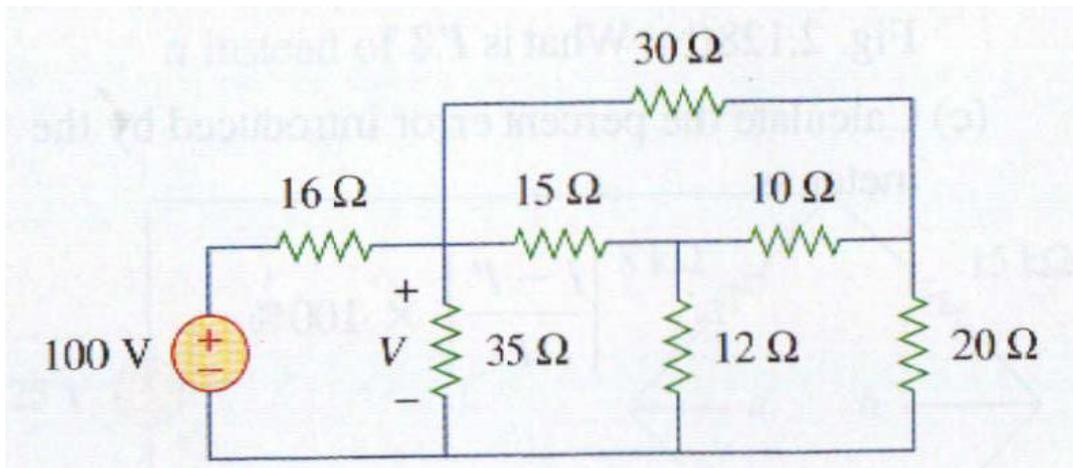

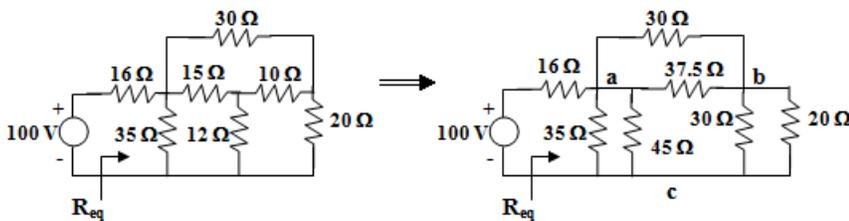We need to find  $R_{eq}$  and apply voltage division. We first transform the Y network to  $\Delta$ .



$$R_{ab} = \frac{15 \times 10 + 10 \times 12 + 12 \times 15}{12} = \frac{450}{12} = 37.5 \Omega$$

$$R_{ac} = 450 / (10) = 45 \Omega, R_{bc} = 450 / (15) = 30 \Omega$$

Combining the resistors in parallel,

$$30 \parallel 20 = (600/50) = 12 \Omega,$$

$$37.5 \parallel 30 = (37.5 \times 30 / 67.5) = 16.667 \Omega$$

$$35 \parallel 45 = (35 \times 45 / 80) = 19.688 \Omega$$

$$R_{eq} = 19.688 \parallel (12 + 16.667) = 11.672 \Omega$$

By voltage division,

$$v = \frac{11.672}{11.672 + 16} 100 = \underline{\underline{42.18 \text{ V}}}$$