
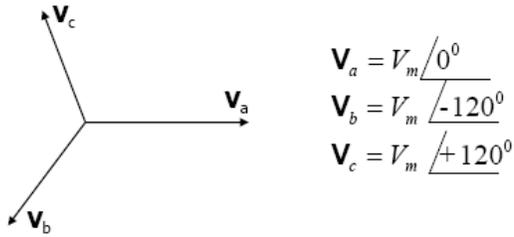


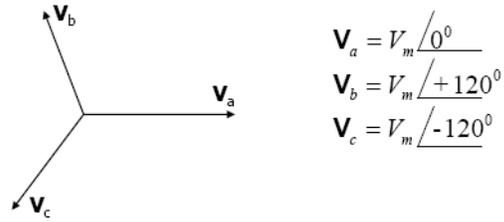**abc (positive) phase sequence:** b-phase lags a-phase by  $120^\circ$ , and c-phase leads a-phase by  $120^\circ$ .




**acb (negative) phase sequence:**




Two Different Three-phase Source configurations:

**Wye (or Y) Connected Source**

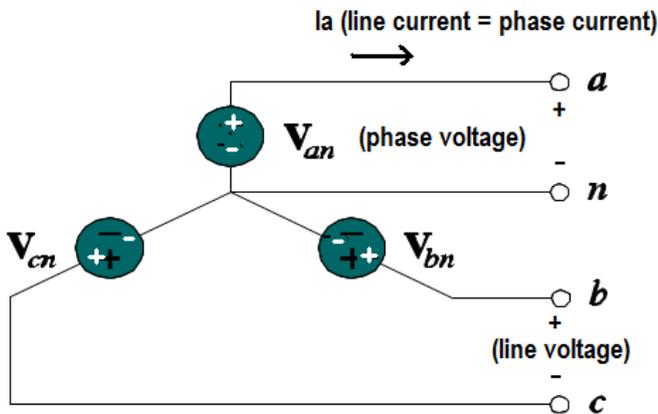

**Delta (or Δ) Connected Source**

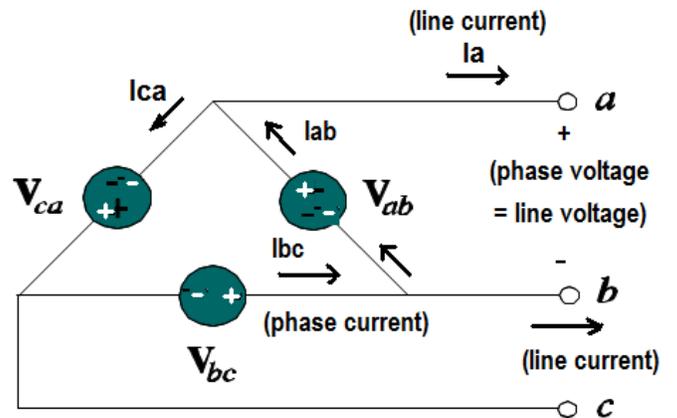


Wye Source (for Load just reverse all currents):

Phase Voltages  $V_{an}, V_{bn}, V_{cn}$

Line Voltages  $V_{ab}, V_{bc}, V_{ca}$

(KVL:)  $V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_{an} \angle +30^\circ$  (abc)  
 $= \sqrt{3} V_{an} \angle -30^\circ$  (acb)

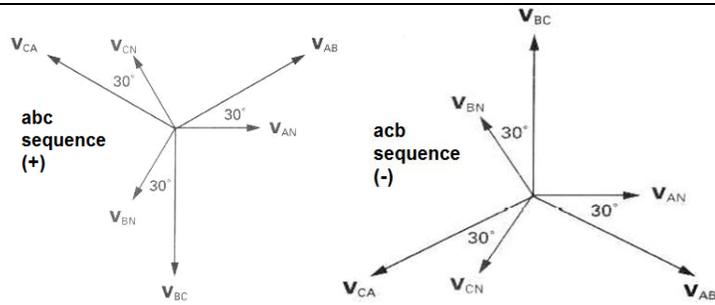Phase Currents and Line Currents are the same  
 $I_a, I_b, I_c$  are phase and line currents



Wye Voltages (abc)

(acb)


Delta Source (for Load just reverse all currents):

Phase Voltages and Line Voltages are the same  
 $V_{ab}, V_{bc}, V_{ca}$  are phase and line voltages

Phase Currents  $I_{ab}, I_{bc}, I_{ca}$

Line Currents  $I_a, I_b, I_c$


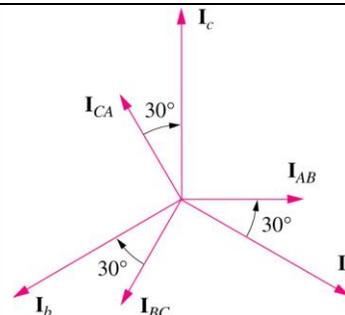
(KCL:)  $I_a = I_{ab} - I_{ca} = \sqrt{3} I_{ab} \angle -30^\circ$  (abc)  
 $= \sqrt{3} I_{ab} \angle +30^\circ$  (acb)




Delta Currents – (abc)

(acb)


Balanced Y-Y Connection:

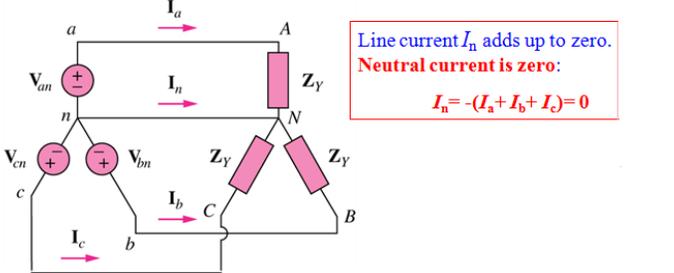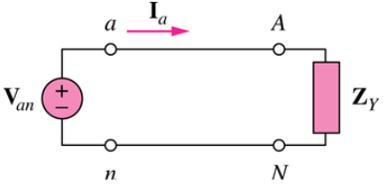	<p>Single Phase Equivalent</p>  <p><math>I_a = V_{an} / Z_Y</math> and all other Voltages and Currents found by using phase relationships above</p>
---	---


Balanced Delta – Delta Connection

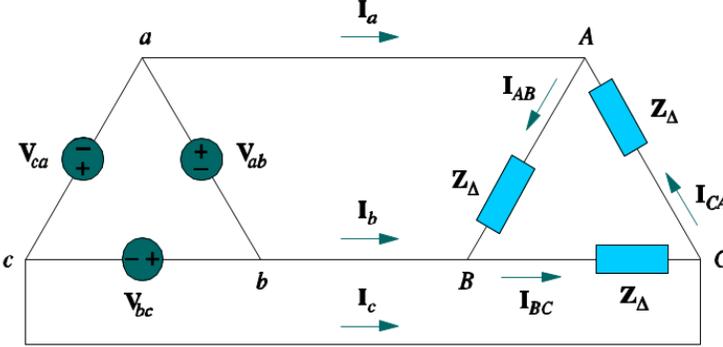	<p><math>I_{ab} = V_{ab} / Z_{\Delta}</math>  <math>I_{bc} = V_{bc} / Z_{\Delta}</math>  <math>I_{ca} = V_{ca} / Z_{\Delta}</math></p> <p>(abc)  <math>I_a = I_{ab} - I_{ca} = \sqrt{3} I_{ab} / \underline{-30}</math> (+30 acb)  <math>I_b = I_{bc} - I_{ab} = \sqrt{3} I_{bc} / \underline{-30}</math>  <math>I_c = I_{ca} - I_{bc} = \sqrt{3} I_{ca} / \underline{-30}</math></p>
---	---

Balanced Wye – Delta Connection

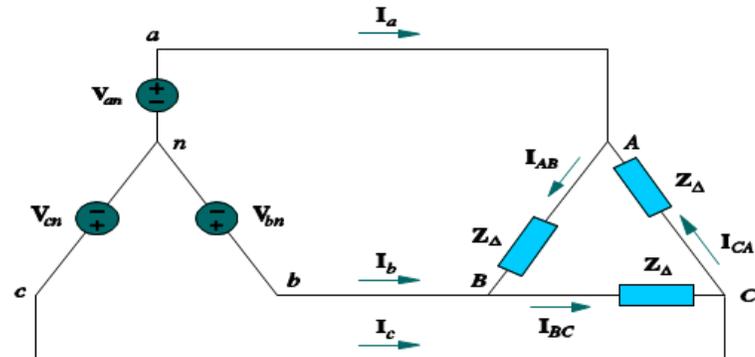	<p><math>I_{ab} = V_{ab} / Z_{\Delta}</math>  <math>I_{bc} = V_{bc} / Z_{\Delta}</math>  <math>I_{ca} = V_{ca} / Z_{\Delta}</math></p> <p>(abc)  <math>I_a = I_{ab} - I_{ca} = \sqrt{3} I_{ab} / \underline{-30}</math> (+30 acb)  <math>I_b = I_{bc} - I_{ab} = \sqrt{3} I_{bc} / \underline{-30}</math>  <math>I_c = I_{ca} - I_{bc} = \sqrt{3} I_{ca} / \underline{-30}</math></p>
---	---

Delta-Wye Conversions: using R below but Z works the same way:

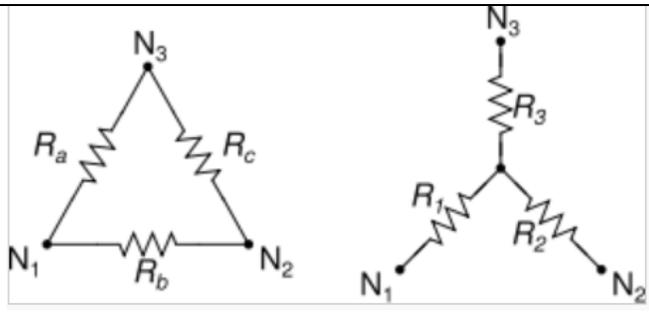	$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$ $R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$ $R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$	$R_1 = \frac{R_b R_c}{R_T}$ $R_2 = \frac{R_a R_c}{R_T}$ $R_3 = \frac{R_a R_b}{R_T}$ <p>where <math>R_T = R_a + R_b + R_c</math></p>
--	---	---

BALANCED: IF  $R_1 = R_2 = R_3 = R_Y$  and  $R_a = R_b = R_c = R_{\Delta}$ , then  $R_{\Delta} = 3R_Y$ , and  $R_Y = R_{\Delta} / 3$